

GATE 2010 EE(40-52)

1

EE24BTECH11030 - J.KEDARANANDA

- 1) A separately excited DC machine is coupled to a 50 Hz, three-phase, 4-pole induction machine as shown in the figure. The DC machine is energized first and the machines rotate at 1600 rpm. Subsequently, the induction machine is also connected to a 50 Hz, three-phase source, the phase sequence being consistent with the direction of rotation. In steady state,


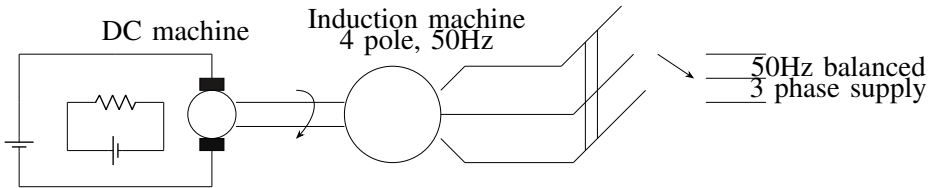
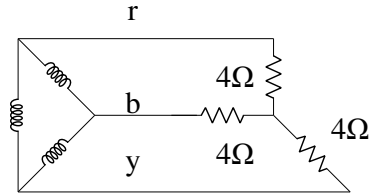
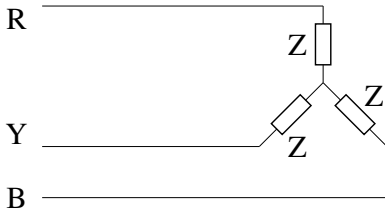



Fig. 1

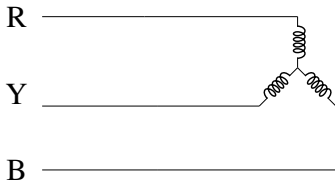- a) both machines act as generators
 - b) the DC machine acts as a generator, and the induction machine acts as a motor
 - c) the DC machine acts as a motor, and the induction machine acts as a generator
 - d) both machines act as motors
- 2) A balanced star-connected and purely resistive load is connected at the secondary of a star-delta transformer as shown in the figure. The line-to-line voltage rating of the transformer is 110 V / 220 V. Neglecting the non-idealities of the transformer, the impedance Z of the equivalent star-connected load, referred to the primary side of the transformer, is:




- a) $3 + j0 \, \Omega$
- b) $0.866 - j0.5 \, \Omega$
- c) $0.866 + j0.5 \, \Omega$
- d) $1 + j0 \, \Omega$

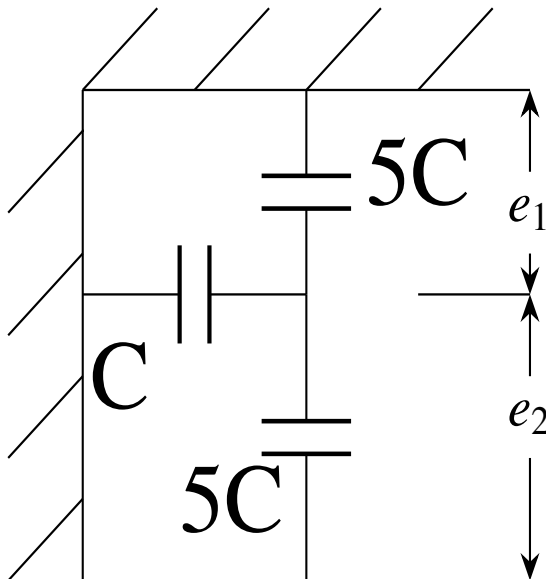- 3) Consider a three-phase, 50 Hz, 11 kV distribution system. Each of the conductors is suspended by an insulator string having two identical porcelain insulators. The self-capacitance of the insulator is 5 times the shunt capacitance between the link and the ground, as shown in the figure. The voltage across the two insulators are:



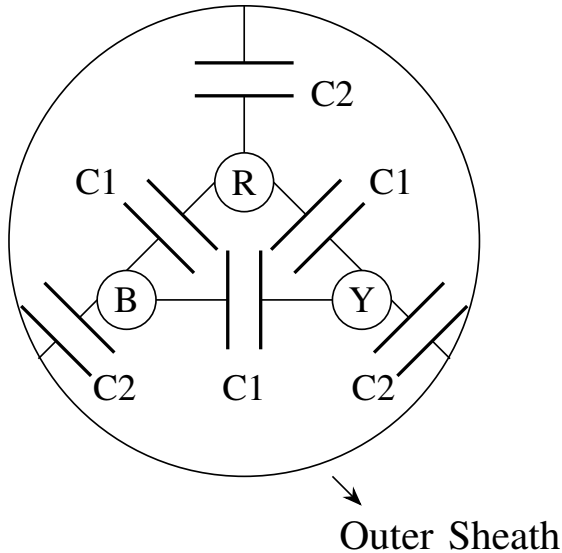- a) $e_1 = 3.74$ kV, $e_2 = 2.61$ kV
b) $e_1 = 3.46$ kV, $e_2 = 2.89$ kV
c) $e_1 = 6.0$ kV, $e_2 = 4.23$ kV
d) $e_1 = 5.5$ kV, $e_2 = 5.5$ kV
- 4) Consider a three-core, three-phase, 50 Hz, 11 kV cable whose conductors are denoted as R, Y, and B in the figure. The inter-phase capacitance (C_1) between each pair of conductors is $0.2 \mu\text{F}$ and the capacitance between each line conductor and the sheath is $0.4 \mu\text{F}$. The per-phase charging current is



- a) 2.0 A b) 2.4 A c) 2.7 A d) 3.5 A

- 5) For the power system shown in the figure below5, the specifications of the components are as follows:

- G_1 : 25 kV, 100 MVA, $X = 9\%$
- G_2 : 25 kV, 100 MVA, $X = 9\%$
- T_1 : 25 kV/220 kV, 90 MVA, $X = 12\%$
- T_2 : 220 kV/25 kV, 90 MVA, $X = 12\%$
- Line 1: 220 kV, $X = 150$ ohms

Choose 25 kV as the base voltage at generator G_1 , and 200 MVA as the MVA base. The impedance diagrams are shown below:



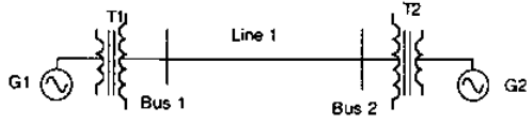



Fig. 5

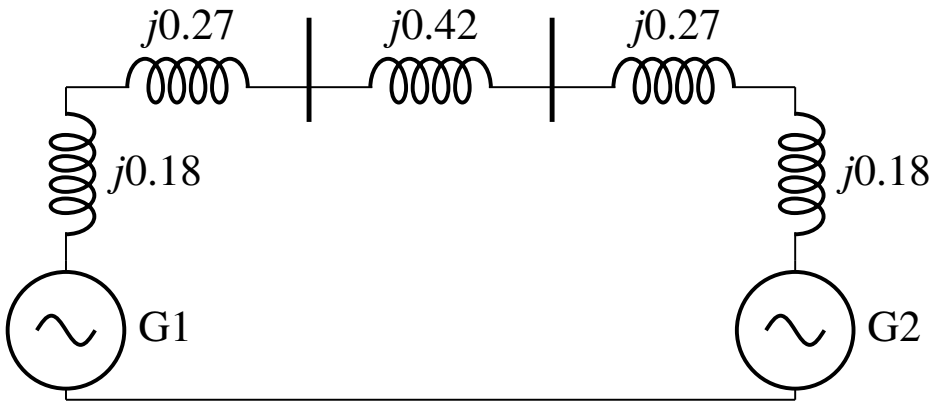


a)

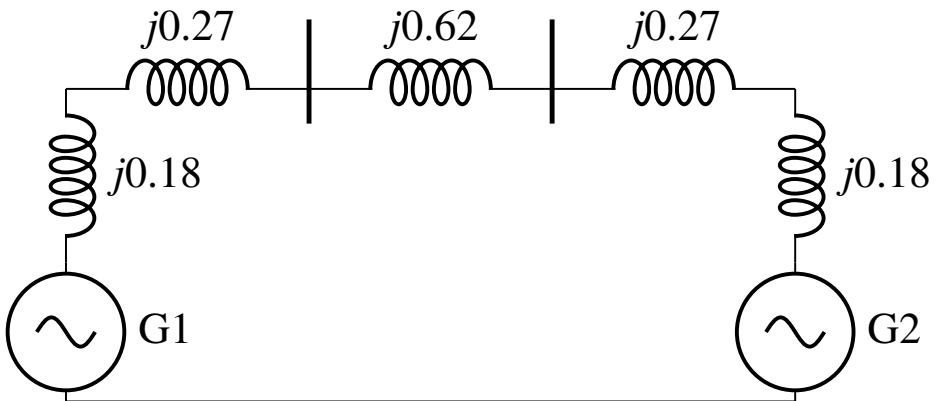

b)

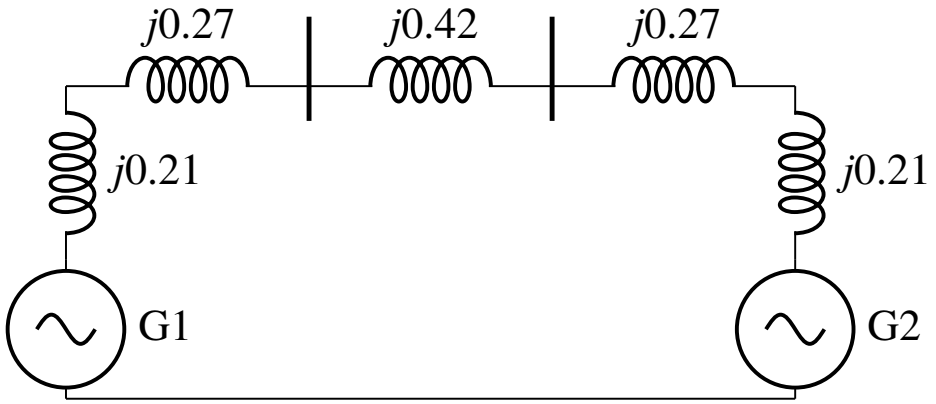


c)

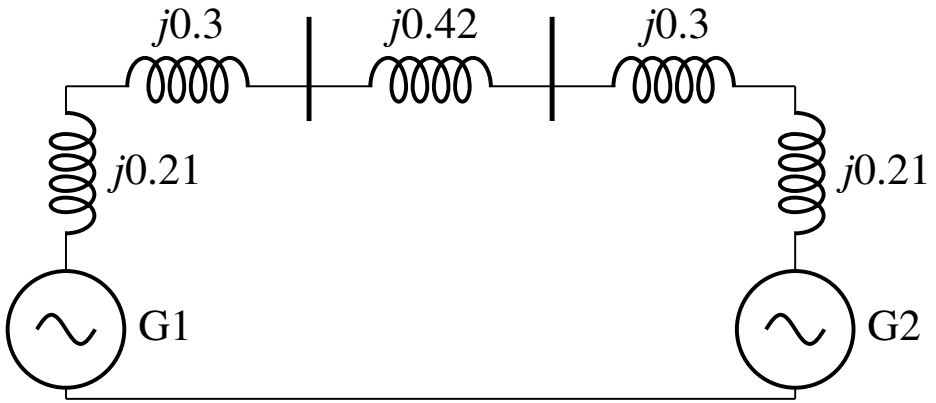

d)

- 6) The TTL circuit shown in the figure 6 is fed with the waveform X (also shown). All gates have equal propagation delay of 10 ns. The output Y of the circuit is

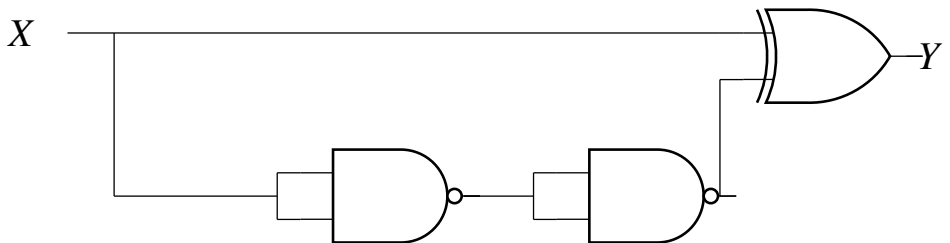



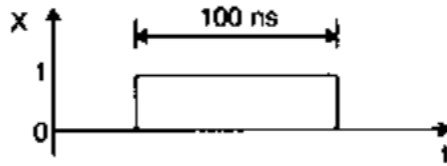



Fig. 6

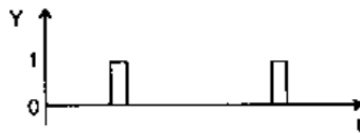


a)

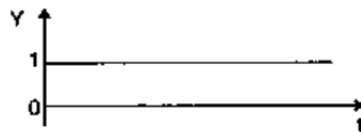

b)

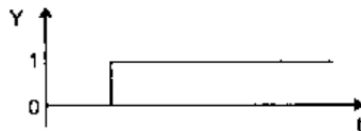

c)

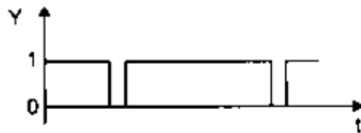

d)

7) When a CALL Addr instruction is executed, the CPU carries out the following sequential operations internally:

- a) (SP) incremented
(PC) \leftarrow Addr
((SP)) \leftarrow (PC)
- b) (PC) \leftarrow Addr
((SP)) \leftarrow (PC)
(SP) incremented
- c) (PC) \leftarrow Addr
(SP) incremented
 \leftarrow (PC)
- d) ((SP)) \leftarrow (PC)
(SP) incremented
(PC) \leftarrow Addr

COMMON DATA QUESTIONS

COMMON DATA FOR QUESTIONS 48 AND 49

A separately excited DC motor runs at 1500 rpm under no-load with 200 V applied to the armature. The field voltage is maintained at its rated value. The speed of the motor, when it delivers a torque of 5 Nm, is 1400 rpm as shown in the figure.7 The rotational losses and armature reaction are neglected.

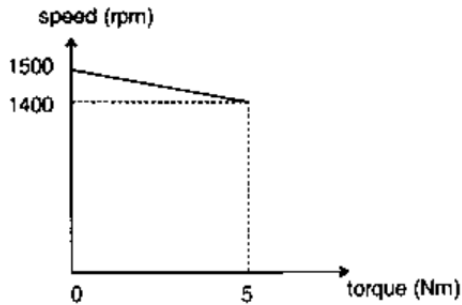


Fig. 7

- 8) The armature resistance of the motor is:
- a) $2\ \Omega$ b) $3.4\ \Omega$ c) $4.4\ \Omega$ d) $7.7\ \Omega$
- 9) For the motor to deliver a torque of 2.5 Nm at 1400 rpm, the armature voltage to be applied is:
- a) 125.5 V b) 193.3 V c) 210 V d) 241.7 V

COMMON DATA FOR QUESTIONS 50 AND 51

Given $f(t)$ and $g(t)$ as shown below:



Fig. 9

10) $g(t)$ can be expressed as

- a) $g(t) = f(2t - 3)$ c) $g(t) = f\left(2 - \frac{3}{2}\right)$
b) $g(t) = f\left(\frac{t}{2} - 3\right)$ d) $g(t) = f\left(\frac{t}{2} - \frac{3}{2}\right)$

11) The Laplace transform of $g(t)$ is

- a) $\frac{1}{s} (e^a - e^b)$ c) $\frac{e^b}{s} (1 - e^{-a})$
b) $\frac{1}{s} (e^a - e^c)$ d) $\frac{1}{s} (e^a - e^c)$

Linked Answer Questions

Statement for Linked Answer Questions 52 and 53:

The following Karnaugh map 11 represents a function F .

		YZ			
		00	01	11	10
X	0	1	1	1	0
	1	0	0	1	0

Fig. 11

12) A minimized form of the function F is

- a) $F = \overline{X}Y + YZ$ c) $F = \overline{X}Y + \overline{Z}$
b) $F = \overline{X}\overline{Y} + YZ$ d) $F = \overline{X}\overline{Y} + \overline{Z}$